

L6 practice problems

- Perform the following unsigned addition operation. The 8-bit unsigned binary inputs are represented in hexadecimal digits.

$$\begin{array}{r}
 1001\ 1111 \\
 + 0100\ 1110 \\
 \hline
 1101\ 1111
 \end{array}$$


9F + 4E

- Assume the hexadecimal digits in Question 1 are 8-bit 2's complement representations of the signed input values.

Give the decimal equivalent of the signed input values and also of the result.

2's complement: 10011111 = -97 01001110 = 78 result = -19

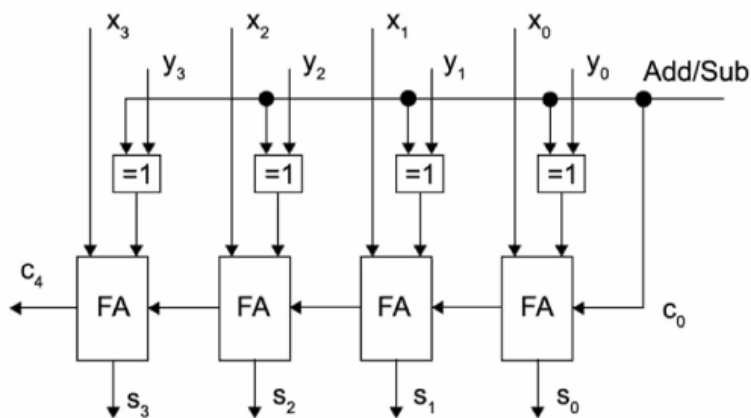- Illustrate how the decimal subtraction (3 - 7) is carried out in the following circuit by indicating the logic level (i.e. 0 or 1) at every input and output (including intermediate signals) on the circuit.



- Draw the diagram of a 6-bit wide 2's complement adder/subtractor circuit using six full adders.